

DC Circuits

Name: _____ Section: 4BL-____ Date performed: ____/____/____

Lab station: _____ Partners: _____

Circuit box # _____

Equivalent resistance

Measurements (include units and uncertainties):

Circuit diagrams

$$R_1 = \text{_____} \pm \text{_____} \quad (\text{range: } \text{_____})$$

$$R_2 = \text{_____} \pm \text{_____} \quad (\text{range: } \text{_____})$$

$$R_3 = \text{_____} \pm \text{_____} \quad (\text{range: } \text{_____})$$

$$R_{\text{ser}} = \text{_____} \pm \text{_____} \quad (\text{range: } \text{_____})$$

$$R_{\text{par}} = \text{_____} \pm \text{_____} \quad (\text{range: } \text{_____})$$

$$R_{\text{cmb}} = \text{_____} \pm \text{_____} \quad (\text{range: } \text{_____})$$

Calculated equivalent resistances:

Discrepancy tests

$$R_{\text{ser}} = \text{_____} \pm \text{_____}$$

$$R_{\text{par}} = \text{_____} \pm \text{_____}$$

$$R_{\text{cmb}} = \text{_____} \pm \text{_____}$$

Show all calculations, including full uncertainty calculations:

Internal resistance

Draw the circuit diagram (include the switch):

R () (range)	V () (range)	I ()
()	()	
()	()	
()	()	
()	()	
()	()	
()	()	
()	()	

R () (range)	V () (range)	I ()
()	()	
()	()	
()	()	
()	()	
()	()	
()	()	
()	()	

Attach V vs. I graph from Excel.

slope = _____ \pm _____ (from linest)

y -intercept = _____ \pm _____ (from linest)

x -intercept = _____ \pm _____ (calculated)

V_{oc} = _____ \pm _____

I_{sc} = _____ \pm _____

R_{int} = _____ \pm _____

R_{lim} = _____ \pm _____ (range:)

R_{bat} = _____ \pm _____